

Analysis And Applications
of
Power Electronics
Converters
(GE-332)

Analysis & App. Of PE Converters (S.K. Singh)
(EE-332)

Page No.: _____

Power Electronics

- Diodes PiN Diodes → Transient Voltage & current
- Power Electronic Devices → Controlled transistors
- IGBT, MOSFET
- Flow to Medium Power ← Voltage Controlled Devices.
- APP.) BJT, Thyristors,
- Current Controlled Devices.
- Very high power App. (HVDC / FACTS)
- AC - DC Controlled Rectifiers
- DC - DC Choppers
- DC - AC Converters
- AC - AC Converters

Applications -

- Photovoltaic Inverters
- Battery Chargers
- HVDC Transmission
- FACTS Devices
- Electric Vehicles

Syllabus

* Unit-I - Analysis of Phase Controlled Converters, Effect of source inductance, Analysis of Inverters, PWM techniques, harmonic reduction, resonant D.C. link Inverter, Analysis of Resonant Converters.

* Unit-II - DC - DC Switched mode Converters, Buck Boost, Buck-Boost, Cuk and bridge converters, Converters with Isolation, flyback, forward, push-pull

Unit III - Switch Mode Power Supplies
Configuration, Regulation, Control Circuits, EMI, HF
transformers, rectifiers & filters. High frequency -
cycloconverters, PWM Rectifier

Unit IV Introduction to ICR, TSC, VAR Compensation, electric
utility applications, industrial industrial applications

→ Books-

(1) Power Electronics Converter Application & Design - by Ned Mohan
Undeland and Robbins

(2) Power Electronics Circuits, Devices & Applications - by
Minkachid.

(3) Fundamentals of Power Electronics - by Robert W. Erickson
& Dragon Maksimovic

(4) Power Electronics by P.C. Sen.

→ Evaluation pattern:-


Midsem - 30%

Assignments - 10%


End Sem - 45%

Lab - 15%

Phase Controlled Rectifier

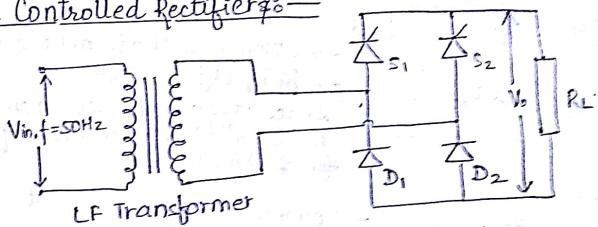

Half Controlled Bridge Rectifier

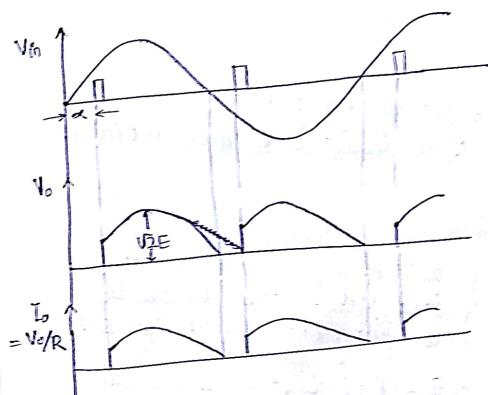

- Centre Tapped Transformer
- ① P.T.V
- ② More no. of turns
- ③ Asymmetry of transformer windings - Harmonics increased.


$$V_o, \text{avg.} = \frac{2\sqrt{2}E}{2\pi} \int_0^{\pi} \sin^2 \omega t \cdot d(\omega t) = \frac{\sqrt{2}E}{\pi} [1 + \cos 2\omega t]$$

$$V_o, \text{rms.} = \left[\frac{1}{\pi} (\sqrt{2}E)^2 \int_0^{\pi} \sin^2 \omega t \cdot d(\omega t) \right]^{1/2} = E \left[\frac{\pi - \alpha + \frac{\sin 2\alpha}{2}}{\pi} \right]^{1/2}$$


Input Power, $P_{in} = E \cdot I_{rms}$ → Input RMS Current

Output Power, $P_o = V_{rms} \cdot I_{rms}$

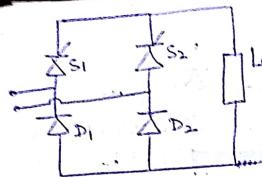
$$\text{Power factor} = \frac{P_o}{P_{in}} = \frac{V_{rms} \cdot I_{rms}}{E \cdot I_{rms}}$$



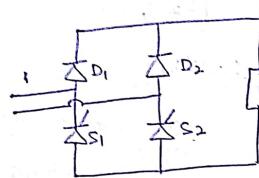→ Common Cathode Arrangement
→ Firing ckt. is simple.
Since they share common cathode,
no isolated firing ckt. is required
for 2 thyristors.



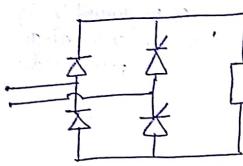
→ Common Anode Arrangement
→ Isolated firing ckt.




→ Isolated firing ckt.
This circuit should be avoided.

For resistive load, the O/P will be same, but w.r.t. the firing ckt., the I & Q ckt. is preferred because it can be triggered by a common firing ckt. for the two SCR's.

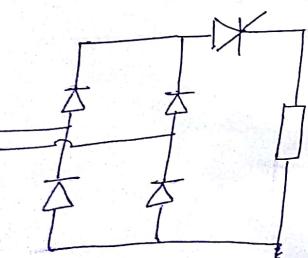
Now, in the case of load $Z = R + j\omega L$, the I & Q ckt. will have the similar problem; due to the inductive load so the heavy current may force the thyristor to conduct.



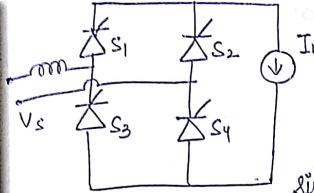
This is a simple one with only one triggering circuit. The resistive load works fine. But for inductive load, we can lose the control & current will circulate. So, not used for inductive load.



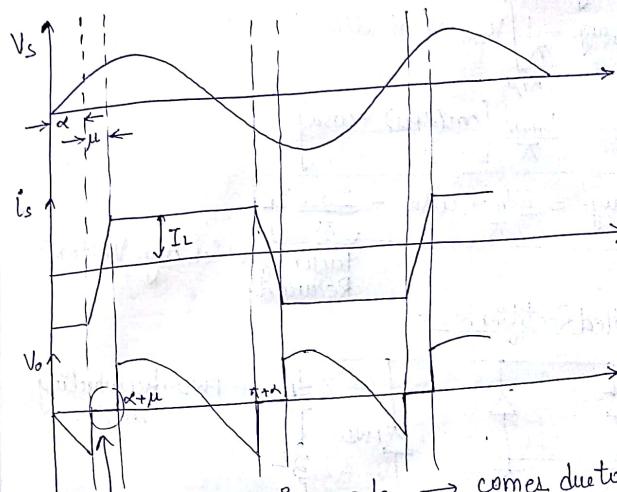L_s = source inductance of Transformer
 I_L = (load) current source.
 μ = overlapping angle, when all the 4 thyristors conduct simultaneously, but there is no short circuit condition.



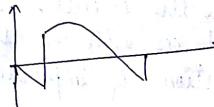due to overlapping angle \rightarrow comes due to the source inductance L_s . If there is no L_s , then the avg. value will increase & V_o will be like —



$$V_o = 0 ; \alpha \leq \omega t \leq \alpha + \mu$$

During commutation,
 $L_s \frac{di}{dt} = V_s = V_{max} \sin \omega t$

Integrating over the commutation interval -

$$\int_{-\pi}^{\pi} d\alpha = \frac{V_{max}}{L} \int_{\alpha/\omega}^{\alpha+\mu} \sin \cot d\alpha$$

$$\cos(\alpha+\mu) = \cos \alpha - \frac{2\omega L}{V_{max}} I_L$$

Avg. O/P Voltage -


$$V_o, \text{avg.} = \frac{1}{\pi} \int_{-\pi}^{\pi} V_{max} \sin \cot d(\cot)$$

$$= V_{max} \left[\cos(\alpha+\mu) + \cos \alpha \right]$$

$$\Rightarrow V_o, \text{avg.} = \frac{2V_{max} \cos \alpha}{\pi} - \frac{2\omega L}{\pi} I_L$$

Factor by which Avg. Voltage is Reduced.

Half Controlled Rectifier -

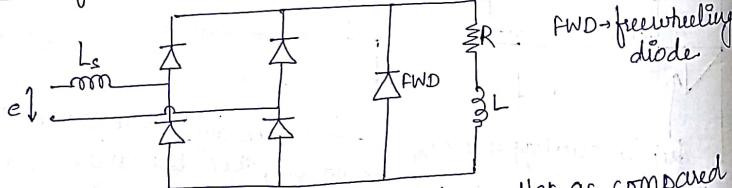


Voltage drop of FWD should be much smaller as compared to other diodes in the circuit. So, FWD takes care of inductive load as well as the effects due to it. Voltage Regulation is improved.

Disadv. → An extra diode is required.

Effect of load Power factor -

Case (i) - Discontinuous load current:-
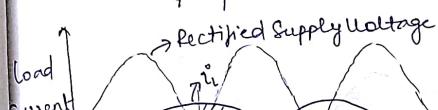
$$\alpha > \phi \text{ and } \beta - \alpha < \pi$$



$$\text{Let supply voltage, } e = \sqrt{2} E \sin(\omega t + \phi) \\ \text{Power factor, } \tan \phi = \frac{\omega L}{R}$$

$$\frac{dI}{dt} + iR = e$$

$$i = \frac{\sqrt{2} E}{Z} \sin(\omega t + \alpha - \phi) + C e^{\omega t / \tan \phi}$$

Steady State Component

Transient Component

for calculating C, the boundary condition is $i=0$ at $\omega t=0$.


$$C = -\frac{\sqrt{2} E \cos \phi}{R} \sin(\alpha - \phi)$$

To find avg. current during α to π , just integrate.

To find the avg. FWD current (during π to β), find the total avg. voltage and divide by R to find total avg. current & subtract the bridge current to find FWD current.

$$\text{Avg. load current, } I_o = \frac{\sqrt{2} E [1 + \cos \alpha]}{\pi R}$$

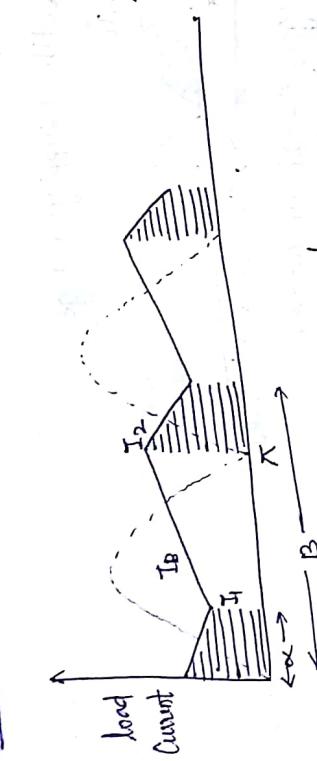Case (ii) Continuous load Current [$\alpha < \beta$ and $\beta - \alpha \leq \pi$]



$$I_1 = \text{Max. Load Current}$$

$$I_2 = \text{Bridge Current (Avg.)}$$

$$I_b = \text{FWD Current (Avg.)}$$

Load Current —

$$i = \frac{\sqrt{2}E}{R} \cos\phi \sin(\omega t + \alpha - \phi) + C e^{-\omega t/\tan\phi}$$

Boundary Condition —

$$I_1 = i \Big|_{\omega t=0} = \frac{\sqrt{2}E}{R} \cos\phi \sin(\alpha - \phi) + C e^{\frac{-\alpha}{\tan\phi}} \quad (1)$$

$$I_2 = i \Big|_{\omega t=\pi-\lambda} = \frac{\sqrt{2}E}{R} \cos\phi \sin(\pi - \alpha - \phi) + C e^{\frac{-(\pi-\alpha)}{\tan\phi}} \quad (2)$$

$$I_1 = I_2 e^{-\alpha/\tan\phi} \quad (3)$$

$$\text{from eq "(1), (2) \& (3)" — } C = \frac{\sqrt{2}E}{R} \cos\phi \left[\frac{\sin\phi e^{-\alpha/\tan\phi} - \sin(\alpha - \phi)}{1 - e^{-\alpha/\tan\phi}} \right]$$

$$\text{Bridge Current, } I_B = \frac{\sqrt{2}E}{R} \cos\phi \left[\sin(\alpha + \lambda - \phi) + \dots \right]$$

$$\text{g. Bridge Current, } I_B = \frac{1}{2} \int_{\alpha}^{\pi-\lambda} I_B d(\omega t).$$

Avg. load Current, $I_o = \frac{\sqrt{2}E}{\pi R} [1 + \cos\alpha]$

$$I_o = I_b - I_B$$

$$\text{Avg. Thyristor Current} = \frac{I_B}{2}$$

Higher Avg. Thyristor Current — Without freewheeling diode.
But we prefer with FWD.

- Q. A single phase half Controlled (semi-Controllable) by connected
to 220V, 50Hz Supply. A load $R=10\Omega$ & connected in
series with a large inductance and load current is ripple free —
determine —
a) the firing angle of commutator
b) Avg. O/P Voltage,

$$V_o = \frac{\sqrt{2}E}{\pi} [1 + \cos\alpha] = 148.62V.$$

$$\text{b) Avg. Load Current, } I_o = V_o/R = 14.862A.$$

- c) DC O/P Power = $V_o I_o = 2208.79W$.
d) RMS O/P Current Voltage,
 $V_{rms} = E \left[\frac{1}{\pi} [\pi - \alpha] + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}}$

$$\text{e) RMS O/P Current, } I_{rms} = I_o = 14.862A.$$

Because of Ripple free (AC component is zero).



f) AC O/P Power = $V_{rms} I_{rms} = 2630.57W$.

g) Rectification efficiency = $\frac{P_{dc}}{P_{ac}} = \frac{2208.79}{2630.57} = 84\%$.




h) Form factor = $\frac{V_{rms}}{V_o} = \frac{17.4}{148.62} = 0.11909$

i) Ripple factor, RF = $\sqrt{P_{ac}^2 - P_{dc}^2}$


Switch Mode Inverters

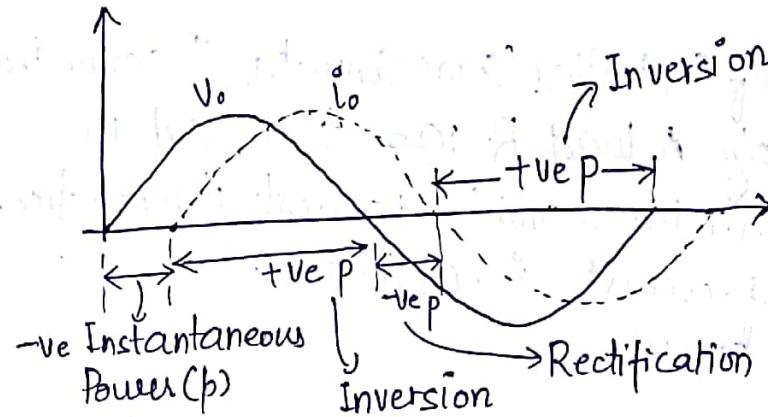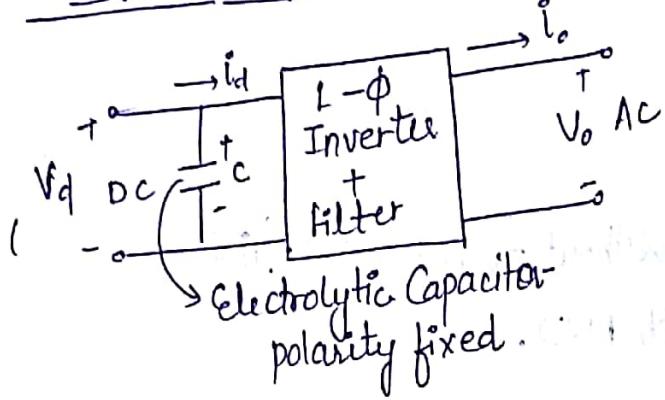

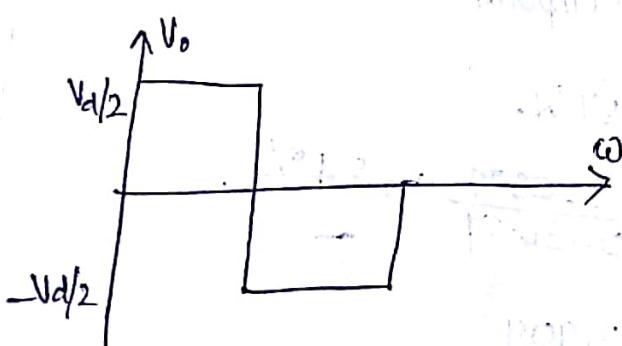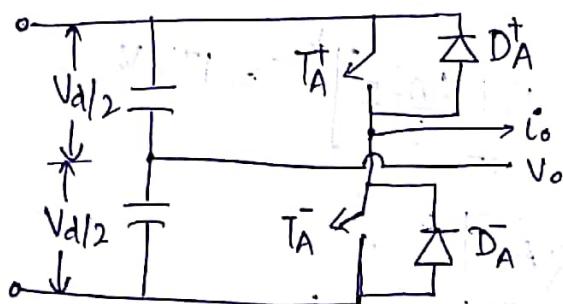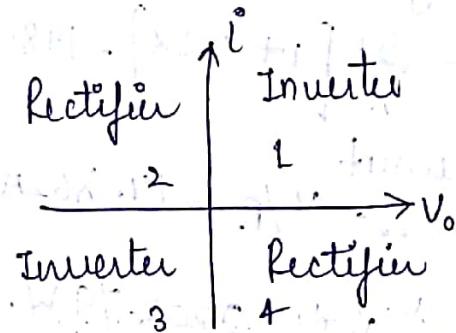Rectification mode
as power flows from O/p to
I/P AC to DC.



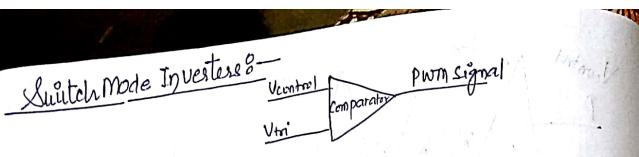- 1) More harmonics
- 2) Energy of square wave > sinus.
- 3) Switching losses small due to less freq.
- 4) Main problem is filter design (size) & heat sinks.




Effect of Modulation Index

$$m_a = \frac{V_{control}}{V_{tri}}$$

$m_a < 1 \rightarrow$ linear operating Region.

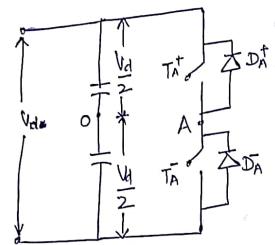$m_a > 1 \rightarrow$ Non-linear op. Reg.




m_f = frequency Modulation Index

$$M_f = \frac{f_{sw}}{f_{control}}$$

$f_{sw} \Rightarrow$ Triangular Carrier Signal

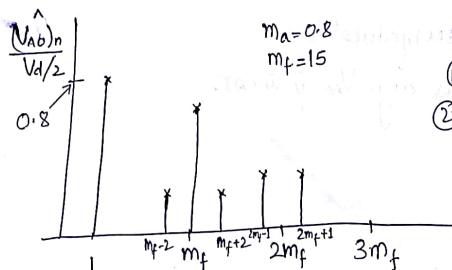m_f \leftarrow Odd (3, 5, ..., 21, ...) Even (X) (Because DC Component will appear. \rightarrow losses will increase.)



$m_f < 21 \rightarrow$ Sub-harmonic components
(Function of fundamental freq)
 \hookrightarrow Synchronous PWM



$\therefore m_f > 21 \rightarrow$ Sub-harmonic negligible
 \star Asynchronous PWM

Dead Time / Blanking time

During this time, the IGBT is dead.

Time required for the switch to go from ON to OFF state.

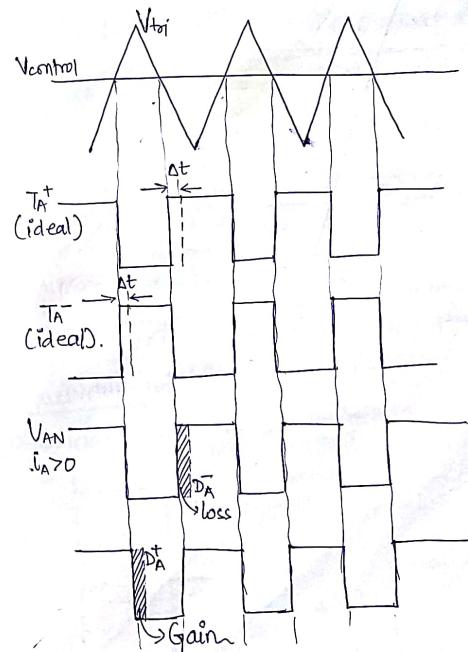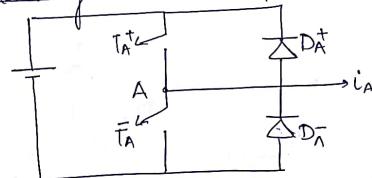Effect of Blanking time on Voltage Source Inverter (VSI) :-



Effect of blanking time on Voltage source Inverter (VSI):

Change in V_{AN} as compared to the ideal case—

$$\frac{V_{AN} - V_{AN}(\text{ideal})}{\text{Blanking time}} = \Delta V_{AN} = + \frac{\Delta t}{T_{SW}} \cdot V_i ; i_A > 0$$


$$= - \frac{\Delta t}{T_{SW}} \cdot V_i ; i_A < 0.$$

Numericals.

Change in V_o —

$$\frac{V_o - V_o(\text{ideal})}{\text{Blanking time}} = \Delta V_o = + \frac{2\Delta t}{T_{SW}} \cdot V_d ; i_o > 0$$

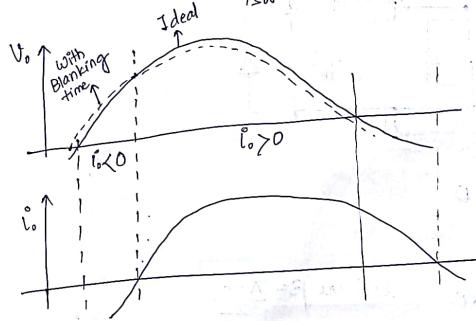
$$= - \frac{2\Delta t}{T_{SW}} \cdot V_d ; i_o < 0.$$




Harmonics $\propto \Delta t$.
So, due to blanking time, some harmonics are introduced.

Square Wave Switching:

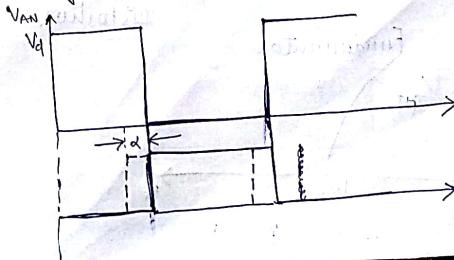Voltage Cancellation Technique ($1-\phi$ inverter).



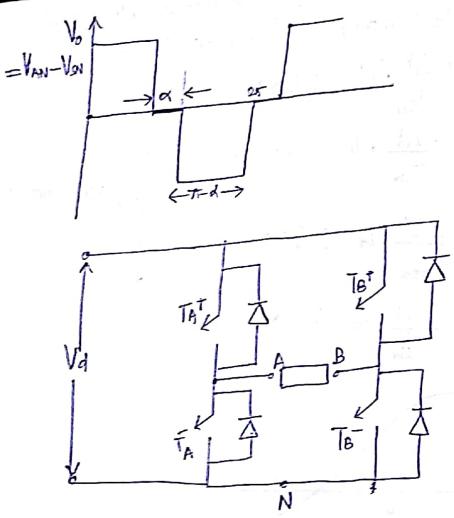


$$(\hat{V}_o)_n = \frac{2}{\pi} \int_{-\pi/2}^{+\pi/2} V_o \cos(n\theta) d\theta$$


$$= \frac{2}{\pi} \int_{-\beta}^{\beta} V_o \cos(n\theta) d\theta \quad \text{where } \beta = \frac{\pi - \lambda}{2}$$

$$= \frac{4}{n\pi} V_o \sin(n\beta)$$
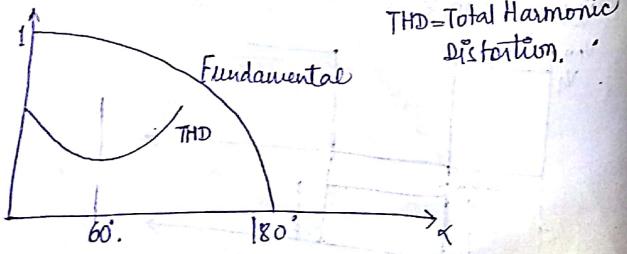
$$(\hat{V}_o)_n = \frac{4}{n\pi} V_o \sin \left[n \left(\frac{\pi}{2} - \frac{\alpha}{2} \right) \right]$$




Notching Technique

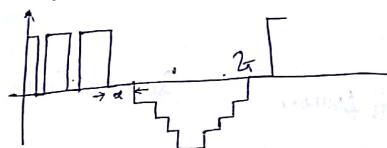


Better Replacement for SPWM.
Bipolar based power system SPWM can't be used with Thyristor.

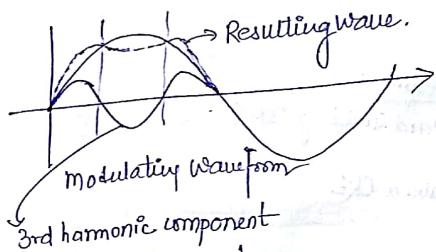
THIPWM \Rightarrow 3-φ Inverter.
Third Harmonic Injection PWM.




Resonant Converters

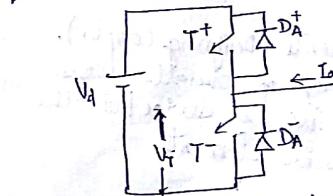

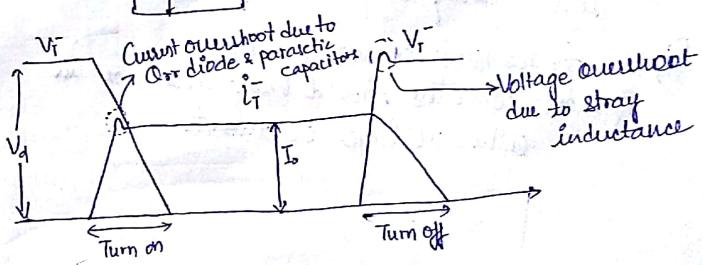- High Switching Losses.
- Higher Switching stress.
- Huge $\frac{di}{dt} + \frac{dv}{dt}$ \Rightarrow Electromagnetic switching noise (EM Induction or EM compatibility)



Earlier Snubber Ckt. was proposed

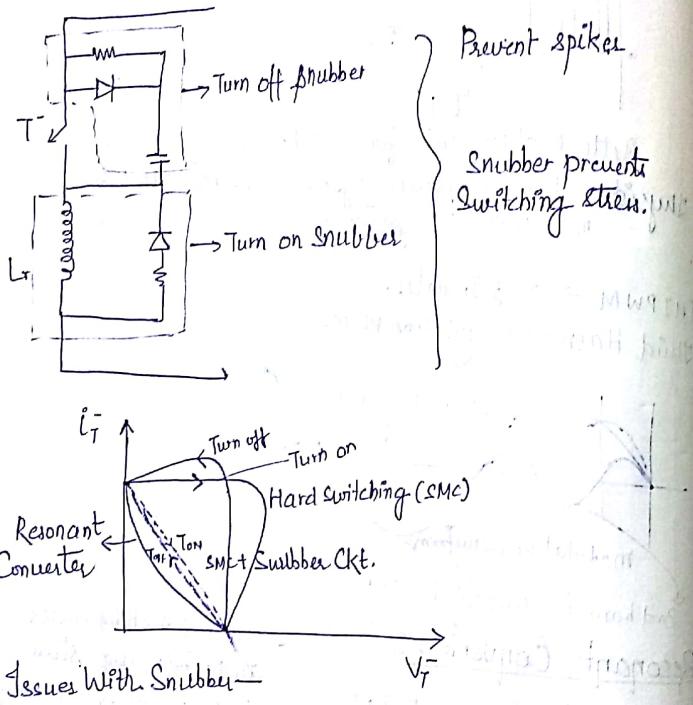

- More no. of electrical components (Designing Complex).
 - Don't get benefit in terms of overall losses.
- Although loss is appearing in device but the loss appears in passive elements.


So, idea for resonant converter comes—
Resonant converter should have resonance in either voltage or current.

— Resonant Converter

→ load
→ switch (Z_{CS}/Z_{VS})
→ DC link

$Z_C/V_S \rightarrow$ zero Current/Voltage switching.

Load Resonant: Class E Inverter

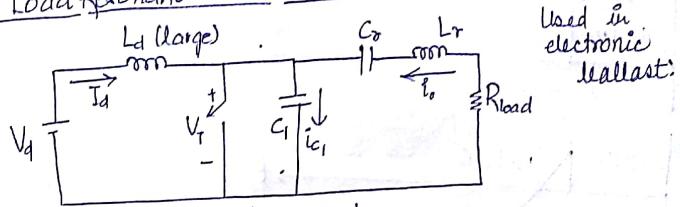


I_d is almost constant.


I_d used to convert voltage source to current source.


Two Modes Of Operation Based On Switchop. 8—

① Turn-ON Mode:

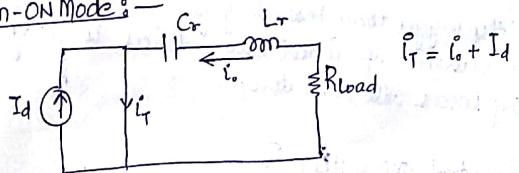

② Turn-Off Mode:

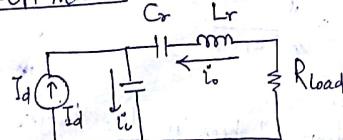

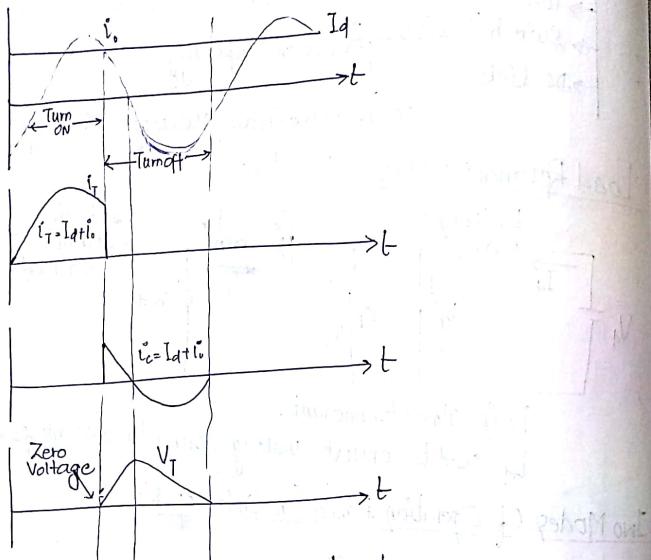

* fsw is slightly bigger than resonating freq.
* the voltage & current of individual devices is going up. Switching losses will come down.

Now how to control o/p Voltage?

fsw → Switching frequency


$$f_r \rightarrow \text{Resonating freq.} = \frac{1}{2\pi\sqrt{L_r C_r}}$$

fsw is slightly less than f_r.

So, we are controlling fsw, & keep it close to f_r, so that current changes & hence gain & then voltage changes.

We are using current source, so that it can boost the o/p Voltage

DC Link Inverter

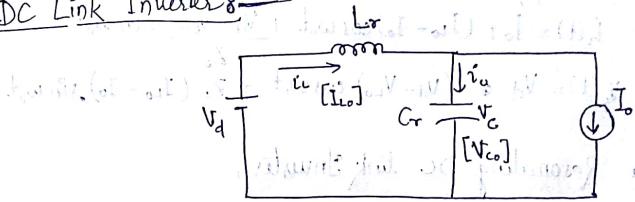

V_{co} → initial cap. voltage at $t=0$.
 I_0 → initial current through inductor at $t=0$.

$$V_c = V_d - L_r \frac{di}{dt} \quad \text{(1)}$$

$$i_L - i_C = I_0 \quad \text{(2)}$$

Differentiate (1) -

$$i_C = C_r \frac{dv_c}{dt} = -L_r C_r \frac{d^2 i_L}{dt^2} \quad \text{(3)}$$

Substituting i_C from (3) to (2) -

$$i_L + C_r L_r \frac{d^2 i_L}{dt^2} = I_0$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{L_r C_r} i_L = \frac{I_0}{L_r C_r}$$

$$\text{or } \frac{d^2 i_L}{dt^2} + \omega_0^2 i_L = \omega_0^2 I_0$$

$$\text{where, } \omega_0^2 = \frac{1}{L_r C_r}; \quad Z_0 = \sqrt{\frac{L_r}{C_r}}$$

Resonating frequency

Characteristic Impedance






Resonant Switch Converters

Zero Current Switching (ZCS)


Initially $i_T = 0$, $V_c = 0$,

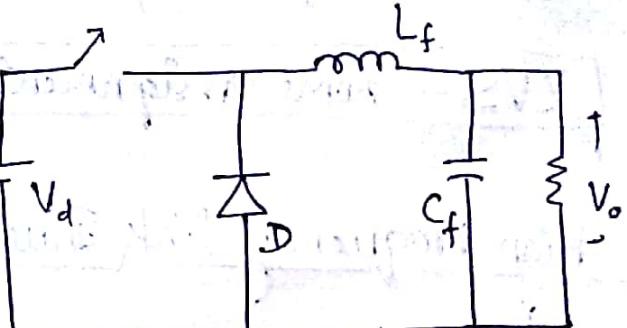load current freewheels through the diode D.




$t_0 < t < t_1$

At $t = t_0$, switch is turned ON.

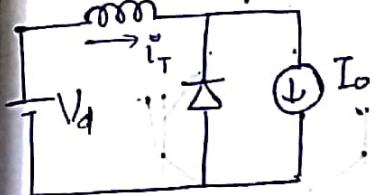



$\rightarrow i_T$ linearly increases.

$\rightarrow V_c \approx 0$.

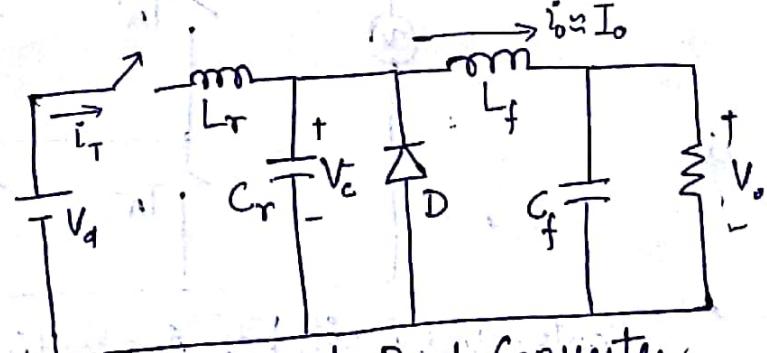


Resonant Buck Converter

$t_1 < t < t_2$

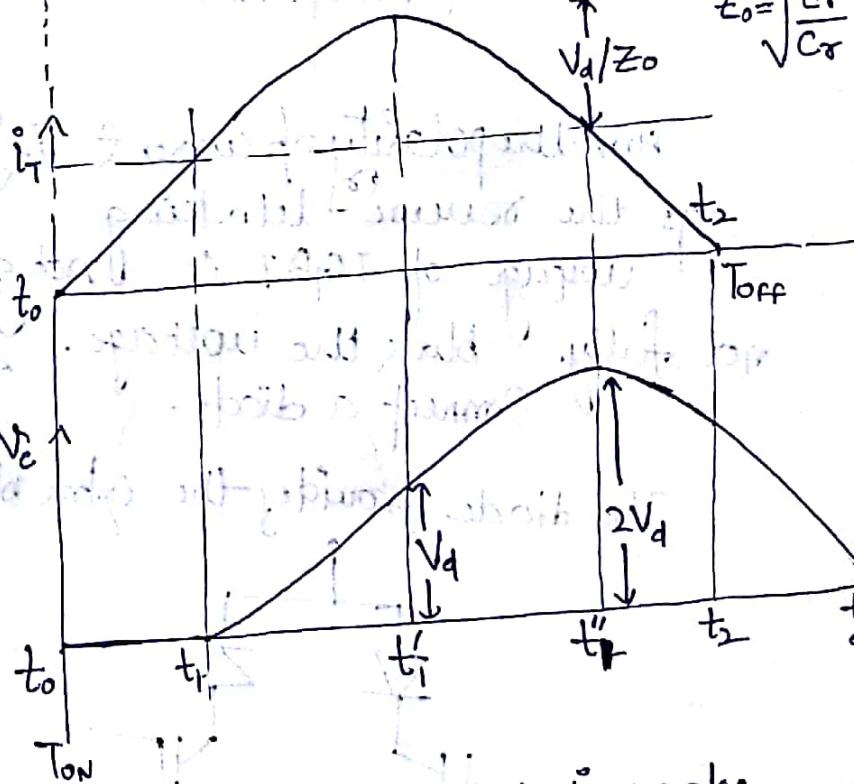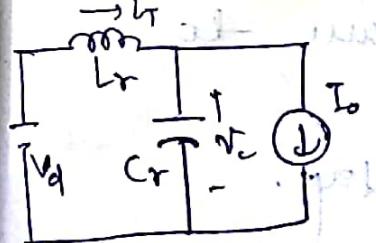

$t_2 < t < t_3$

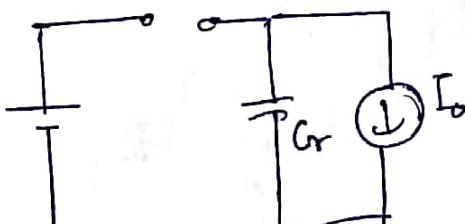

$\rightarrow V_c$ discharges through load.

$$t_1 = t_1' \quad V_c = V_d ; \quad i_T \text{ peaks}$$


$$t_1 = t_1'' \quad i_T = I_o ; \quad V_c = 2V_d$$

$$t_1 = t_2 \quad i_T = 0.$$

T_{sw} - time period from one low to another.

ZVS - zero voltage switching

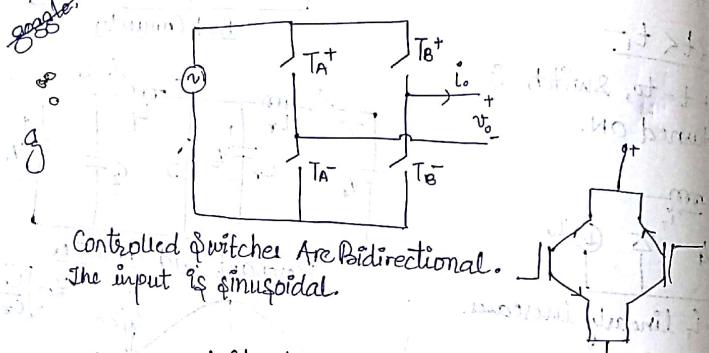
High frequency link Inverter (CycloConverter)






Controlled switches are bidirectional.
The input is sinusoidal.

But the polarity of current is fine.
As the reverse blocking voltage of IGBT is not good so it can not fully block the voltage. So we have to connect a diode.

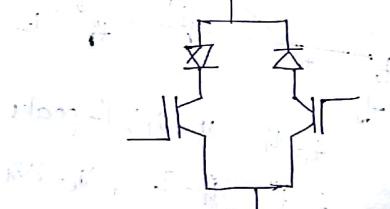The diode provides the extra blocking voltage



Alternatively we can design as -

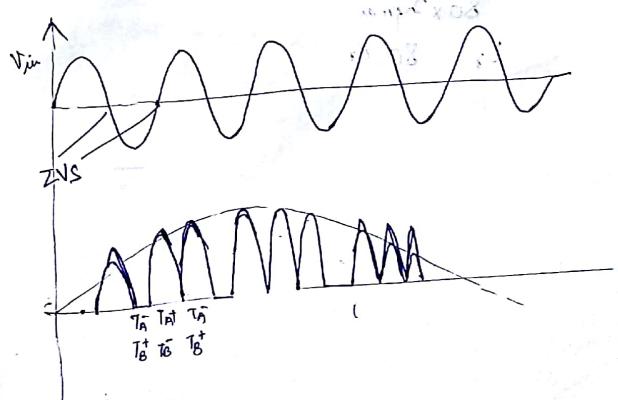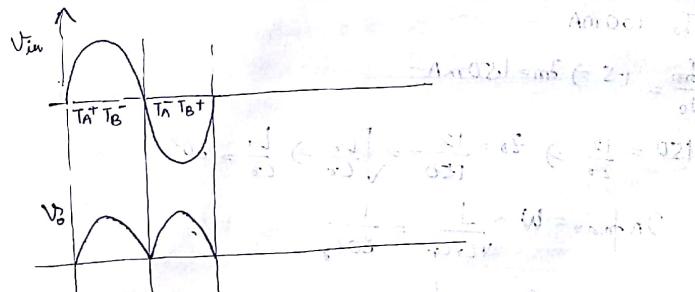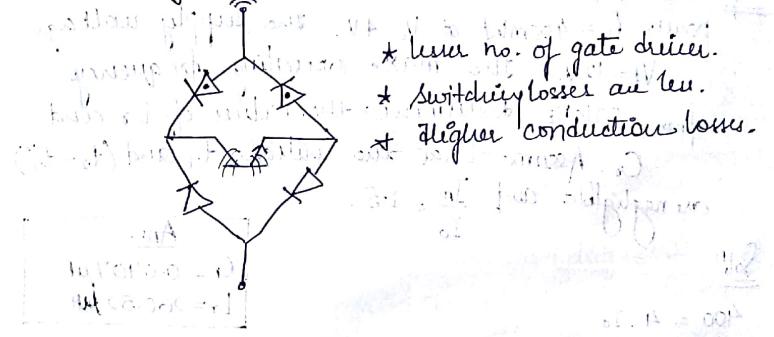

Q. The ZCS Resonant Converter delivers a maximum power $P_L = 400\text{mW}$ at $V_o = 4\text{V}$. The supply voltage $V_d = 12\text{V}$. The max. operating frequency $f_{\max} = 50\text{kHz}$. Determine the values of L_r and C_r . Assume that the initial t_1 and $(t_2 - t_1)$ are negligible and $\frac{I_m}{I_o} = 1.5$.

Soln

$$400 = 4 \cdot I_o$$

$$I_o = 100\text{mA}$$

$$\frac{I_m}{I_o} = 1.5 \Rightarrow I_m = 150\text{mA}$$

$$150 = \frac{12}{Z_o} \Rightarrow Z_o = \frac{12}{150} = \sqrt{\frac{L_r}{C_r}} \Rightarrow \frac{L_r}{C_r} = 80^2$$

$$2\pi f_{\max} = W = \frac{1}{\sqrt{L_r C_r}} = \frac{1}{80 C_r}$$

$$C_r = \frac{1}{80 \times 2\pi f_{\max}}$$

$$L_r = 80^2 \cdot C_r$$


Ans.

$$C_r = 0.0407\mu\text{F}$$

$$L_r = 260.52\mu\text{H}$$

DC-DC SWITCH MODE CONVERTERS

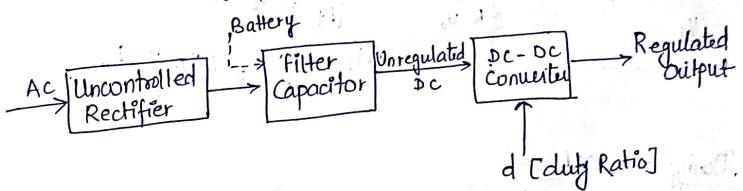Non-Isolated — High frequency / low freq. transformer is absent.




Regulated O/P \Rightarrow it can be varied as per need.

for the constant O/P Voltage & to accomodate change in load, we control the duty ratio.


Non-Isolated

- Buck
- Boost
- Buck-Boost
- Cuk
- Full Bridge



Buck Converter

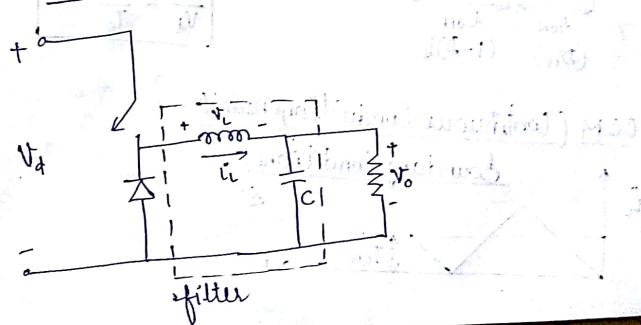


During turn ON :-

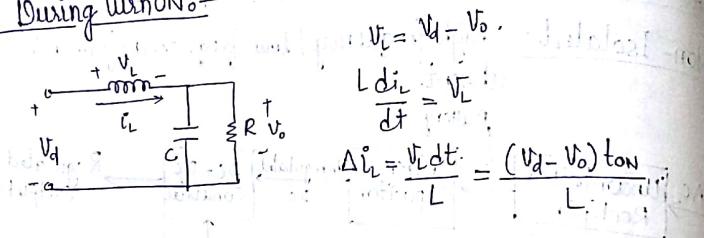

During turn OFF :-

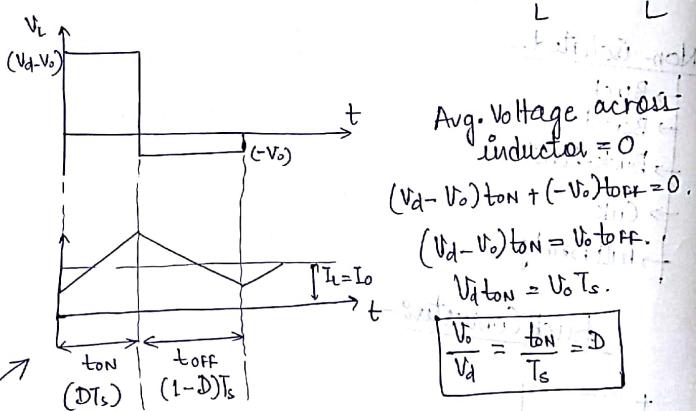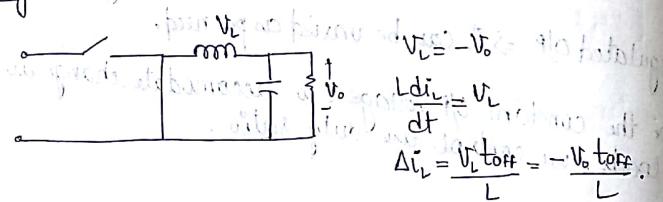


CCM (Continuous Conduction Mode) :-

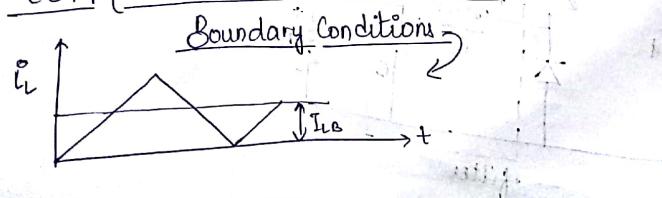


$$I_{LB} = I_{LB} = \frac{1}{2} \hat{i}_L = \frac{(V_d - V_o) D T_s}{2L} = \frac{V_d T_s D (1-D)}{2L}$$

$$I_{LB,max} = \frac{V_d T_s}{8L}$$

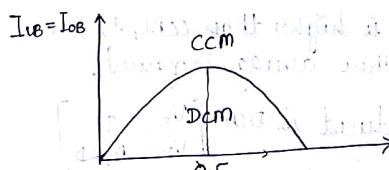

DCM (Discontinuous Conduction Mode) :-

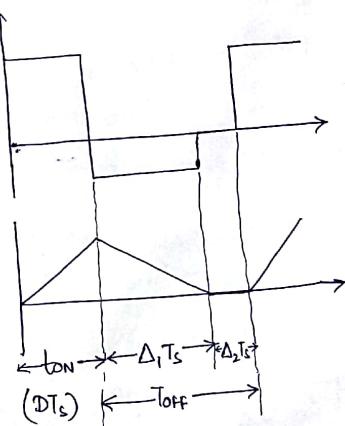

$$(V_d - V_o)t_{on} + (-V_o)\Delta_1 T_s = 0$$

$$(V_d - V_o)D T_s = V_o \Delta_1 T_s$$

$$\frac{V_o}{V_d} = \frac{D}{D + \Delta_1}$$

Power loss negligible,

$$\frac{I_o}{I_0} = \frac{1}{D}$$


CCM

$$\frac{I_o}{I_0} = \frac{D + D_1}{D}$$

DCM

- Under DCM, peak current is higher than CCM, so the current rating is high. [when average is same].
- Some non-linearity is introduced in DCM. $\left[\frac{V_o}{V_D} = \frac{D}{D+D_1} \right]$ because of the above eqn. So, design problem.
- H.W. Derive the same for boost & buck-boost converter.

Output Voltage Ripple :-

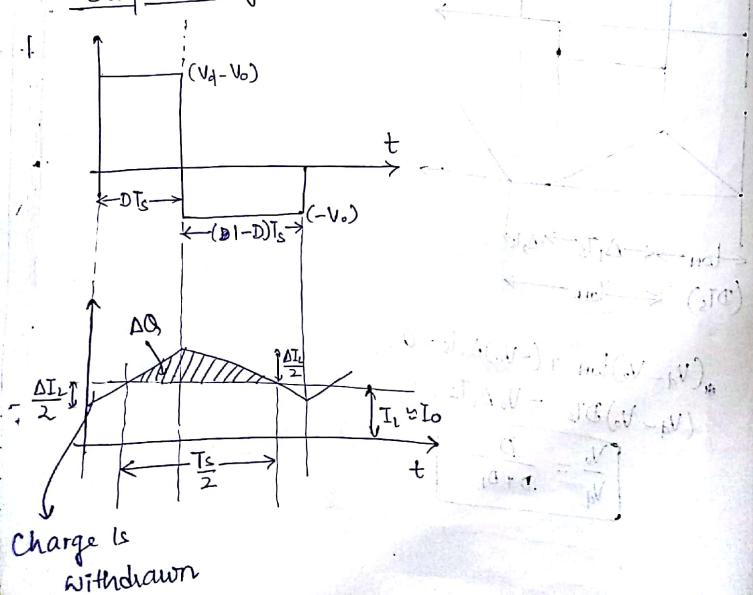

During Turn-OFF :-

$$\frac{L \Delta I_L}{(1-D)T_s} = V_o$$

$$\Delta I_L = \frac{V_o(1-D)T_s}{L}$$


$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{2C} \frac{T_s}{2} \frac{\Delta I_L}{2}$$

$$\Rightarrow \frac{\Delta V_o}{V_o} = \frac{1}{2} \frac{T_s}{2} \frac{(1-D)T_s}{2LC}$$


$$\Rightarrow \frac{\Delta V_o}{V_o} = \frac{\pi^2}{2} (1-D) \left(\frac{f_c}{f_s} \right)^2 ; f_c = \frac{1}{2\pi LC} ; f_s = \frac{1}{T_s}$$

Cut-off frequency
(freq. at which gain comes down by 63.7%)
So, during designing, f_s is constant; f_c & D are varied according to requirement.

Buck-Boost :-

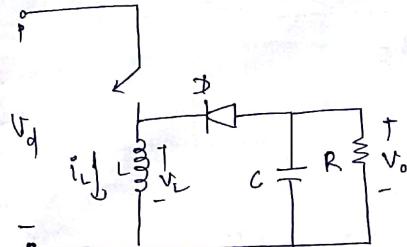

During Turn ON :-

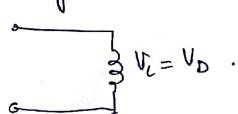


$$\Delta i_L = \frac{V_L dt}{L} = \frac{V_d t_{on}}{L}$$

Cuk Converter (Buck-Boost Converter)

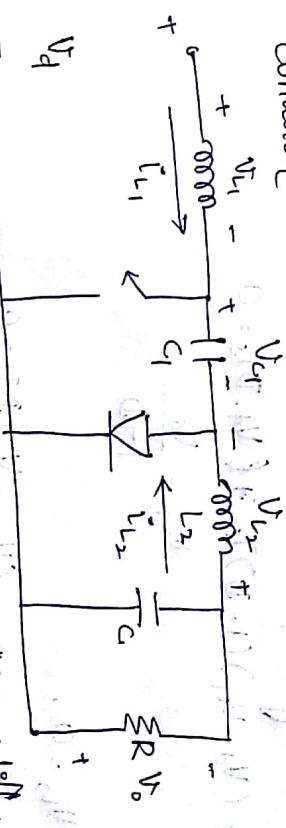
Problems With Buck-Boost

- ① Input & Output Grounds are different.
- ② Initial charging of the capacitor is required.
- ③ Because of the switch, the input current is discontinuous. So, we require a pulsating input current which reduces the life of the source & also the converter.



Here, also the input & output grounds are different.

Turn-Off

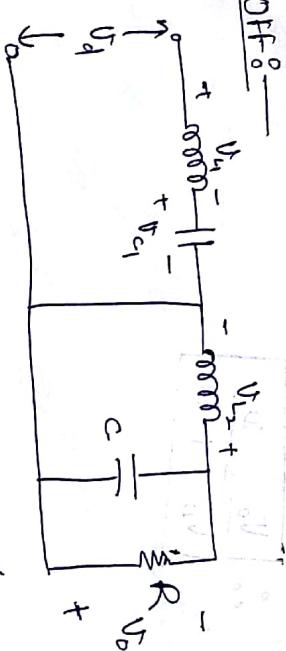

Initially, avg. voltage across $L_1 \& L_2 = 0$.


$$V_{L_1} = V_d - V_{C_1}$$

$$V_{L_2} = -V_o$$

But, we have some voltage across C_1 .

$$V_{C_1} = V_d + V_o$$

Turn-ONs

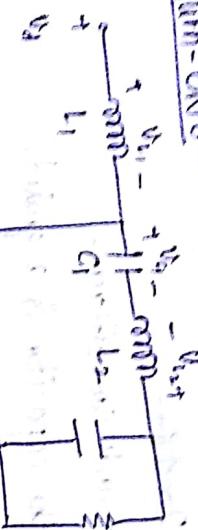

$$V_{d1} = V_d - V_0$$

$$V_{d2} = V_d - V_0$$

$$\text{Avg. } V_{d1} = 0$$

$$\Rightarrow (V_d - V_0)(1 - D)T_s + (V_{d1} - V_0)D T_s = 0$$

$$V_{d1} = \frac{V_d}{1 - D}$$

$$\text{Avg. } V_{d2} = 0$$

$$\Rightarrow (V_d - V_0)(1 - D)T_s + (V_{d2} - V_0)D T_s = 0$$


$$V_{d2} = \frac{V_d}{1 - D}$$

Cuk Converters

Characteristics - Buck-Boost

- * Continuous input and output current. (+)
- * Output is of negative polarity. (-).
- * C_1 acts as a primary means of storing & transferring energy.
- * C_1 or should carry large ripple current.
- * less ripples in U_{d1} and U_{d2} , hence reduced filtering is required.

Full Bridge DC-DC Converter

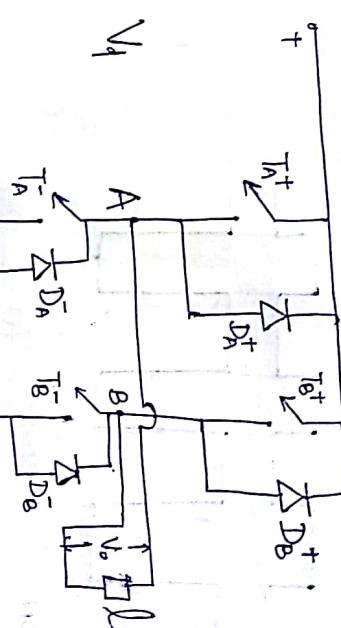


$$\therefore \frac{V_0}{V_d} = \frac{D}{1-D}$$

It's a voltage source converter bcoz no inductor at source. It can not be a boost converter bcoz we do not have energy storing elements.

It's bidirectional in terms of both current & voltage.
four quadrant Application

AC-DC converter following
 $V_o = V_d - V_0$

Unipolar PWM

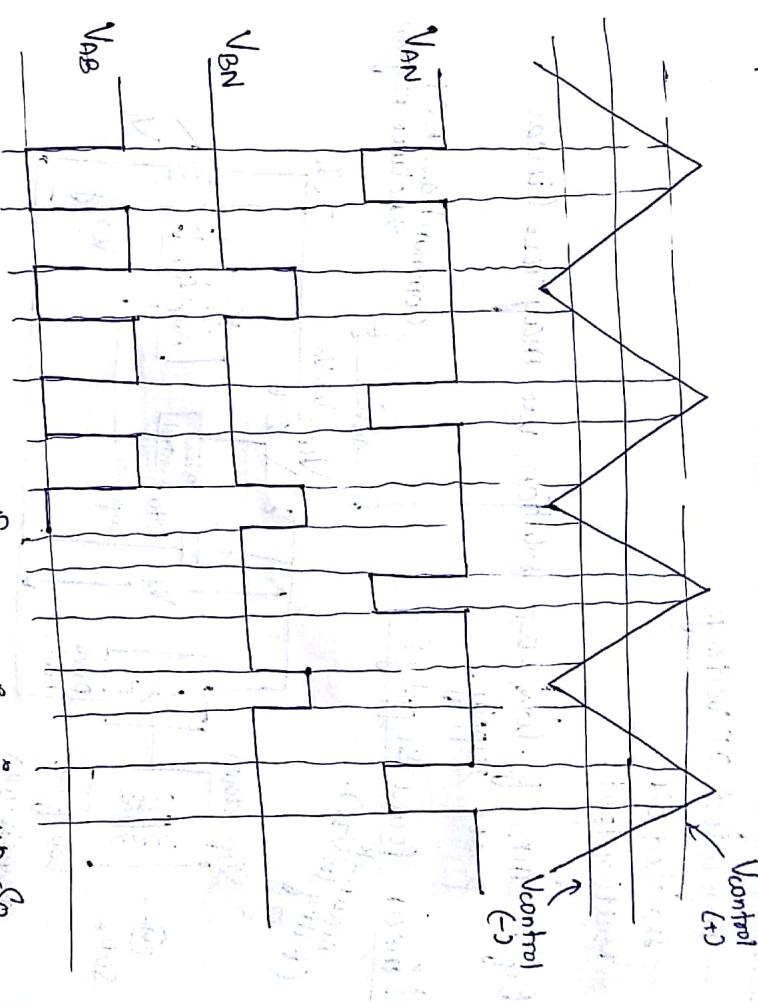

The change is that the ripple frequency is going up. So,

$$D_i = \frac{1}{2} \left(1 + \frac{V_{\text{control}}}{V_{\text{ctrl}}} \right)$$

$$D_2 = D_1 - 1$$

$$V_o = (2D_1 - 1) V_d$$


- Gesamt-Summe
Gesamtbilanzierung
(Abschlusssumme)*

Switching DC Power Supplies

- Regulated O/P voltage.
- Isolated O/P.
- Multioutput.

Before SMPS, for low cost solution, we may use linear power supply.

Linear Power Supply :-

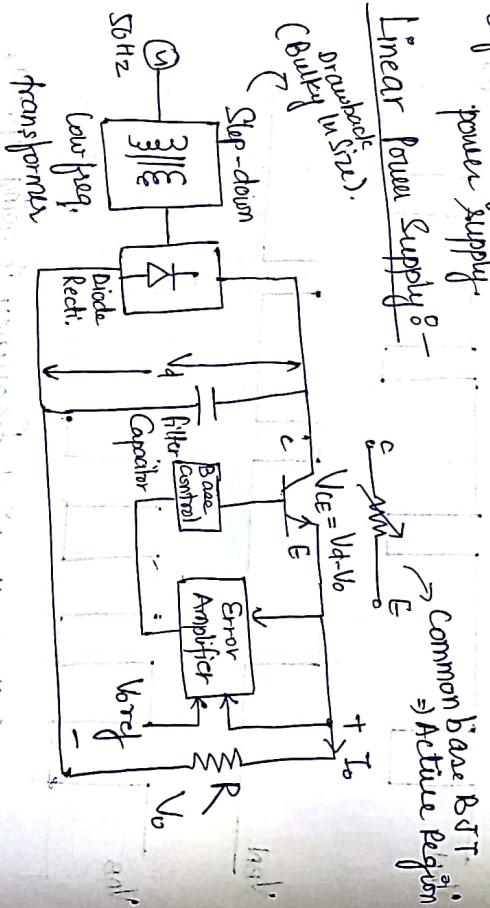

- * Bulky Power Supply.
- * Low efficiency.

- * Advantages
- * EMI issues are negligible.
- * Diodes are not contributing in hard switching.


- * Applications
- * Medical Equipment (noise is avoided).
- * Audio Amplifier.

Low freq. transformer → ferromagnetic core
Permeability is high.

$$\mu_r (\text{low freq.}) \approx 3000,$$

$$\mu_r (\text{high freq.}) \ll \mu_r (\text{low freq.})$$

Switch Mode Power Supply (SMPS)

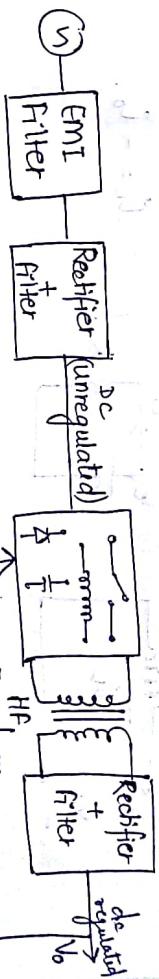


Advantages

- * 70-90% efficiency.
- * HF transformer is compact.
- * Heat sink of reduced size.
- * Life of system gets affected (reliability affected).

Limitations

- * EMI Problem
- * More no. of elements →

Boundary Conditions Of Boost Converter

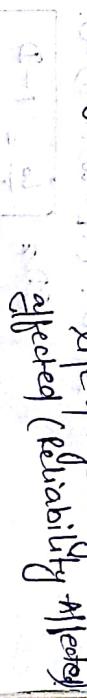

- * During Turn Off :-

$$V_L - V_d = V_o = 0$$

$$\Rightarrow V_L = V_d = V_o$$

Turn ON

$i_o = -i_b$



$$V_d - V_i = 0 \Rightarrow V_d = V_i.$$

$$I_{oB} = (1-D) I_{LB} \rightarrow \text{By Avg.}$$

$$I_{oB} = \frac{I_s \cdot V_o}{2L} D(1-D)^2$$

$$\frac{V_o}{V_d} = \frac{1}{1-D}$$


From $\frac{V_o}{V_d} = \frac{1}{1-D}$, we get $D = \frac{1 - V_o/V_d}{1 - V_o/V_d + 1} = \frac{V_o/V_d}{2 - V_o/V_d}$.

$$\text{At turn-off: } V_d = 0 \Rightarrow V_i = 0. \quad \text{At turn-on: } V_d = V_o(1-D).$$

$$V_d = V_o(1-D) \quad \text{and} \quad V_i = V_o D(1-D) T_s.$$

$$V_d + V_i = V_o(1-D) + V_o D(1-D) T_s = V_o(1-D)(1+DT_s) = V_o(1-D)(1+D) = V_o D + (V_o - V_o D)(1-D) = 0.$$

$$\frac{i_o}{i_b} = \frac{1}{1-D}$$

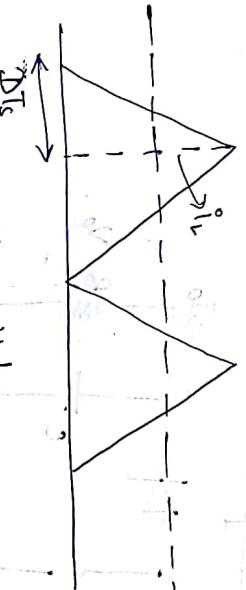

$$\text{slope} = V_o/L T_s.$$

$$i_o = \frac{V_o}{L} D T_s$$

By averaging-


$$I_{oB} \cdot T_s = \frac{1}{2} i_b T_s$$

$$I_{oB} = \frac{1}{2} i_b$$

$$I_{oB} = \frac{1}{2} i_b$$

$$I_{oB} = \frac{V_o}{2L} D T_s$$

$$V_d = V_o(1-D)$$

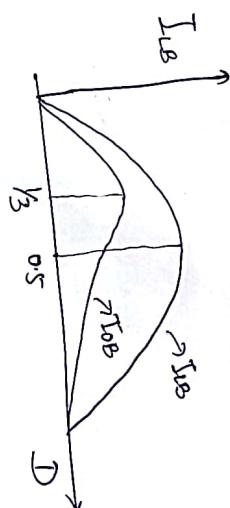

Q: In a boost converter, the duty ratio is adjusted to regulate the output voltage V_o at 48V. The input voltage varies from 12 to 36V. The maximum power output is 50kW. The converter operates in DCM at $f_{sw} = 50\text{kHz}$. Assuming ideal components & C must large, calculate the maximum value of L that can be used.

$$I_o = \frac{P_o}{V_o} = 9.5A.$$

$$I_{oB} = \frac{T_s \cdot V_o}{2L} D(1-D).$$

Point C will be chosen to be in DCM to make $2.5A$ to be its value.

$$\therefore D = 0.75.$$

$$L = \frac{2 \times 10^{-5} \times 48}{2 \times 2.5} \times \left(\frac{3}{64}\right) = 9 \mu H$$

